

Tutorial Sheet-3 (Three Phase Networks)

1. A high-voltage generator is connected to a 3-phase wye connected load through a transmission line. Each phase of the line has impedance Z_l , and the load is a balanced wye with branch impedance Z . Line to line voltage, $|V_{ab}| = 45\text{kV}$, $Z_l = (0.5 + j3) \Omega$, $Z = (4.5 + j9) \Omega$. Find the line currents, power consumed by the load and line losses. Draw the phasor diagram.

[Ans. $I_a = 2\angle -67.38^\circ \text{ A}$, $I_b = 2\angle 172.62^\circ \text{ A}$, $I_c = 2\angle 52.62^\circ \text{ A}$, $P_{load} = 53.99 \text{ MW}$, $P_{line} = 6 \text{ MW}$]

2. A balanced 3-phase a-b-c system with line-to-line voltage $V_{ab} = 208\angle 0^\circ \text{ V}$ supplies to a balanced Δ connected load of 3 kW with a power factor of 0.8 (lag) through ideal conductors. Find the line currents. Draw the phasor diagram.

[Ans. $I_a = 10.41\angle -66.9^\circ \text{ A}$, $I_b = 10.41\angle 173.1^\circ \text{ A}$, $I_c = 10.41\angle 53.1^\circ \text{ A}$]

3. A balanced 3-phase delta connected load of 160 kW , connected to a balanced line voltage of 1100 V , 50 Hz , takes a leading current of 100 A . Find the circuit elements of the load per phase.

[Ans. $R_{ph} = 16 \Omega$, $C_{ph} = 307.87 \mu\text{F}$]

4. Calculate the value of X_C in Fig. 1 such that the combined circuit behaves as a three-phase balanced resistive network. [Ans. 37.5Ω]

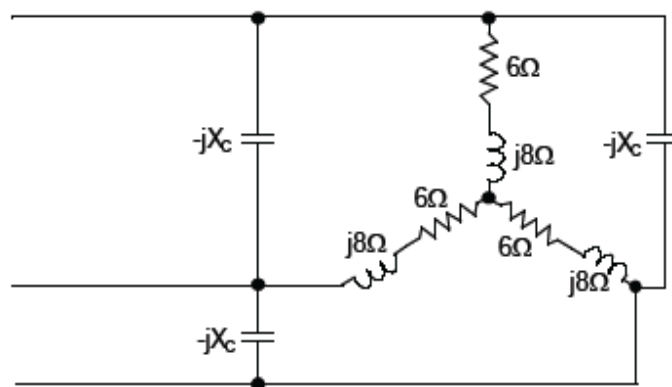


Fig.1

5. For the 3-phase balanced system of Fig.2 calculate the current phasors I_{R1} and I_{R2} as marked in the figure with R-phase supply voltage as reference (sequence be RYB). Each $Z=10\angle 30^\circ \Omega$ and each $Z_1=30\angle -90^\circ \Omega$.

[Ans. $I_{R1}=23.094\angle -30^\circ \text{ A}$, $I_{R2}=23.094\angle 30^\circ \text{ A}$]

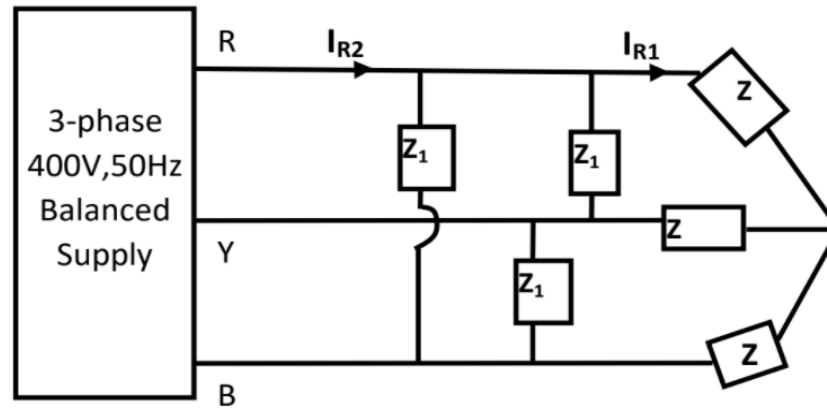


Fig. 2.

6. For the circuit shown in Fig. 3, calculate the branch currents of the Δ connected load and the active and reactive power consumed by it.

[Ans. $I_{RB}=5.75\angle -30^\circ \text{ A}$, $I_{BY}=5.78\angle 90^\circ \text{ A}$, $I_{RY}=5.78\angle 30^\circ \text{ A}$, $P=499 \text{ W}$, $Q=499 \text{ VAR}$]

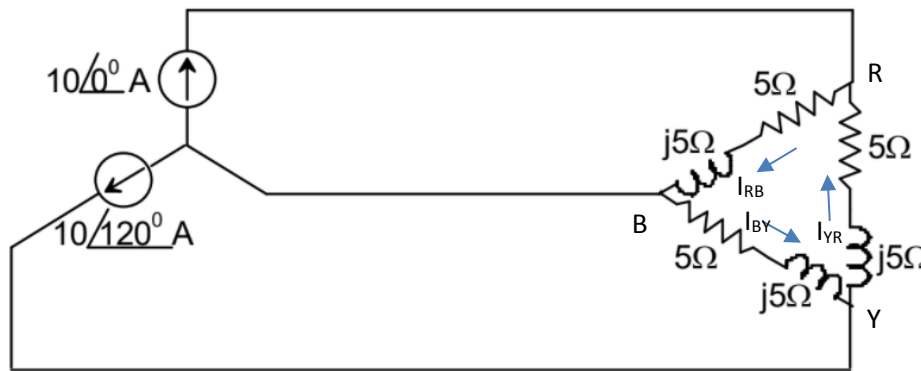


Fig. 3.

7. In the circuit of Fig. 4, A three phase balanced voltage source is supplying power to a three-phase load as shown in Fig. 3. Calculate the line currents.

[Ans. $I_a=41.55\angle -44.86^\circ \text{ A}$, $I_b=41.55\angle -164.86^\circ \text{ A}$, $I_c=41.55\angle 75.14^\circ \text{ A}$]

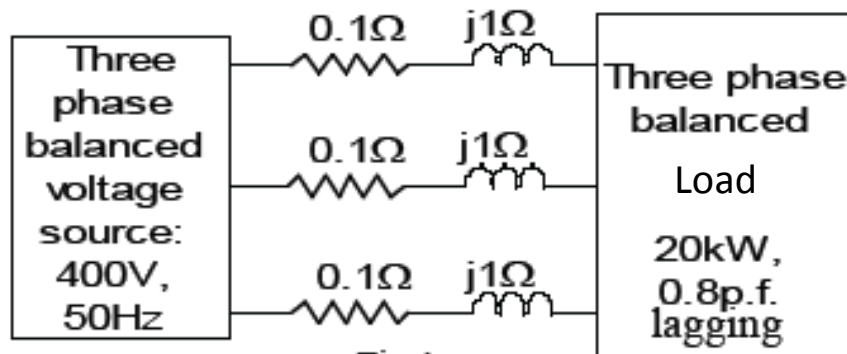


Fig.4

8. A wattmeter reads 5.54 kW when its current coil is connected in R phase and its voltage coil connected between the neutral and the R phase of a symmetrical 3-phase system supplying a balanced load of 30 A at 400 V. What will be the reading on the instrument if the connections to the current coil remain unchanged and the voltage coil be connected between B and Y phases? Take phase sequence RYB. Draw the corresponding phasor diagram. [Ans. 7.2 kW]

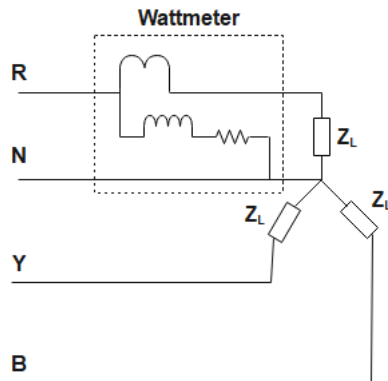


Fig. (a)

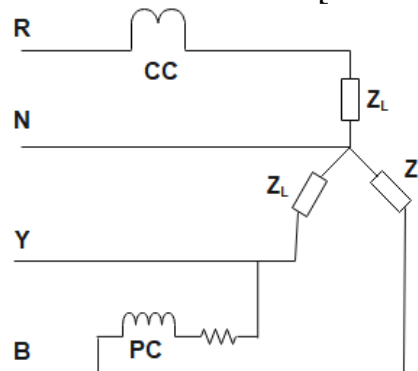


Fig. (b)

9. Calculate the readings of the two wattmeters (W1 and W2) connected to measure the total power for a balanced delta-connected load fed from a three-phase, 400 V balanced supply with phase sequence as R-Y-B as shown in Fig.5. The load impedance per phase contains capacitive reactance, $X_c=14\ \Omega$ and resistance, $R=14\ \Omega$. [Ans. W1 = 13.52 kW, W2 = 3.623 kW]

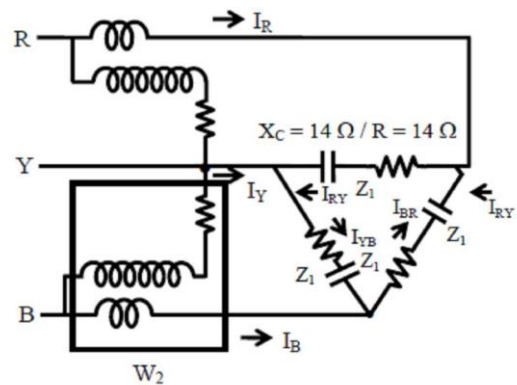


Fig. 5

10. Figure 6 shows a balanced 3-phase, 3 wire system with positive phase sequence. Let $\bar{V}_{BC} = 120\angle 60^\circ$ V and $R_W = 0.6 \Omega$. If the total load (including wire resistance) draws 5 kVA at p.f.= 0.8 lag, find (a) the total power loss in the wire resistance, (b) \bar{V}_{an} .

[Ans: 823.56 W, $78.96\angle 143.47^\circ$]

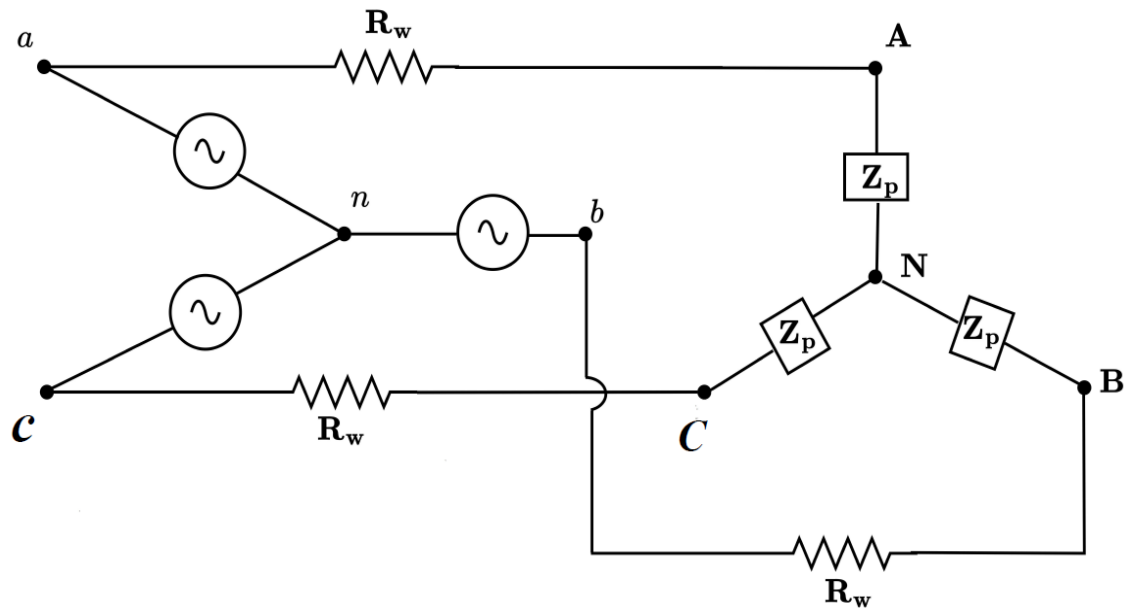


Fig. 6