

ET Tutorial Sheet 1

1. Use mesh analysis to find i_x in the circuit shown in Fig. 1.

[Ans: **3.71 A**]

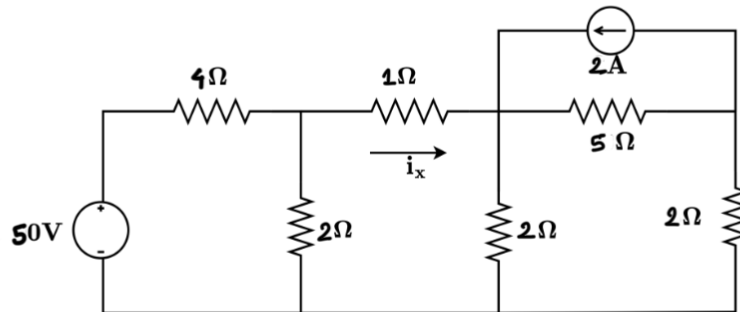


Fig. 1

2. Determine the amount of power delivered/received by the voltage source and the current source in the circuit of Fig. 2.

[$P_{3V} = 1.5 \text{ W}$, $P_{2A} = 17 \text{ W}$]

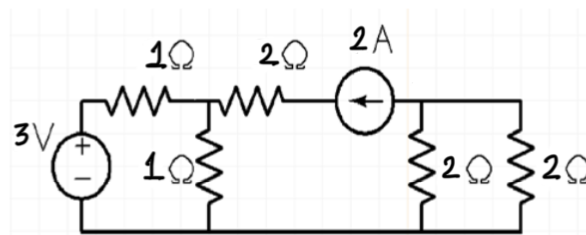


Fig. 2

3. Determine the voltage V_x in the circuit shown in Fig. 3 using node analysis. [Ans: $V_x = 4 \text{ V}$]

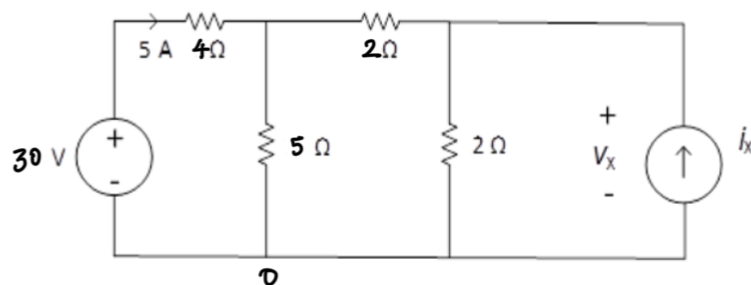


Fig. 3

4. Calculate the value of I_1 of Fig. 4 using (a) Mesh Analysis and (b) Node Analysis. [Ans: $i_1 = 0.329 \text{ A}$]

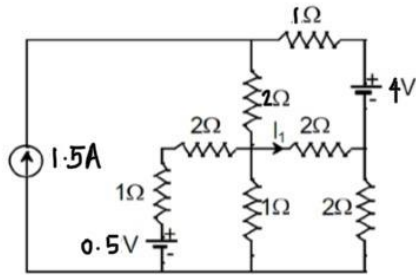


Fig. 4

5 . Use superposition theorem to find the value of V_x in the circuit shown in Fig. 5. [Ans: 11.666 V]

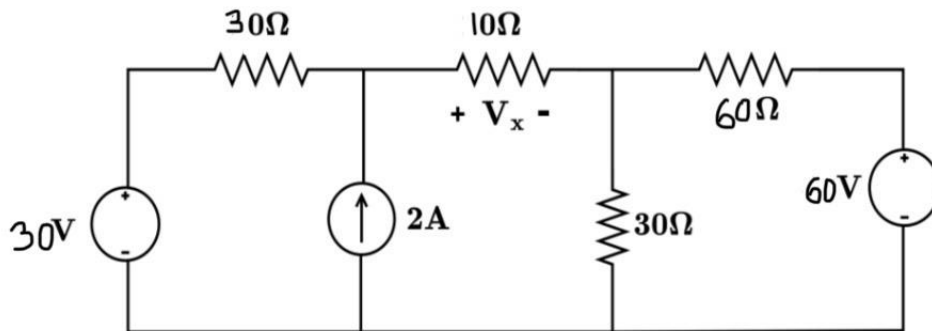


Fig. 5

6. In the circuit of Fig. 6, use Norton theorem to evaluate V_x . [Ans: 114 V]

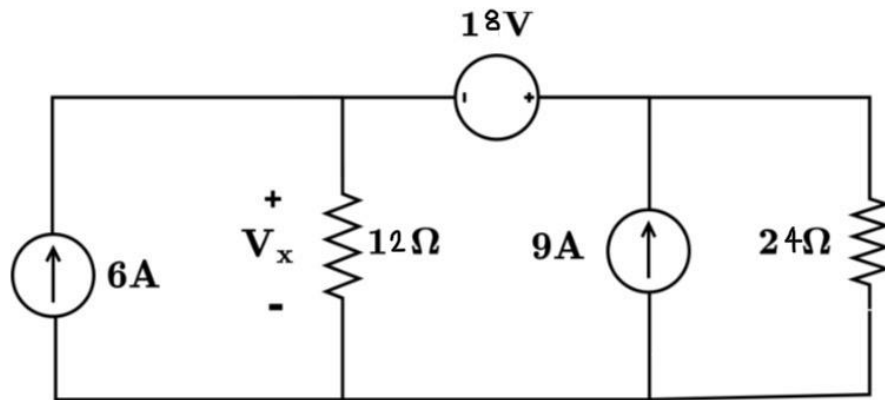


Fig. 6

7. Find the Thevenin equivalent voltage as viewed by the resistance R in the circuit shown in Fig. 7. Find the value of R for maximum power dissipation in it.

[Ans: $R_{th}=15\ \Omega$, $V_{th}=45V$, $R=15\ \Omega$]

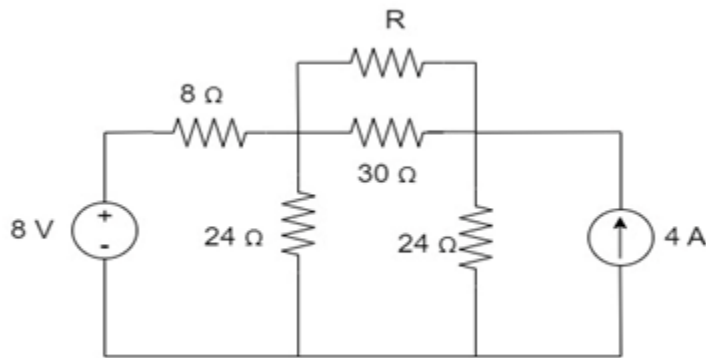


Fig.7

8. In the circuit shown in Fig. 8, find current i_x using (a) mesh analysis, (b) Thevenin theorem. [Ans:-1.43 A]

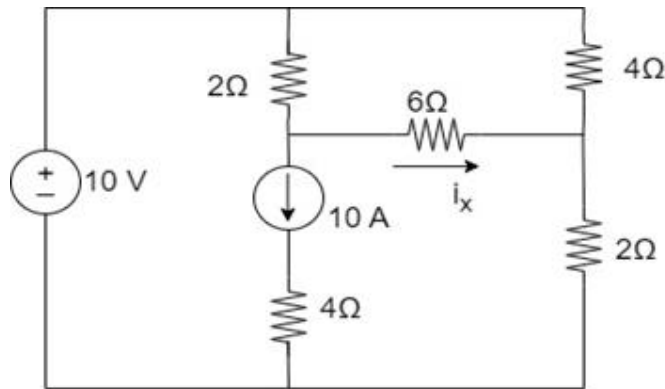


Fig.8

9. In the circuit shown in Fig. 9, what is the maximum power that could be dissipated in R_L ? [Ans: 21.77 W]



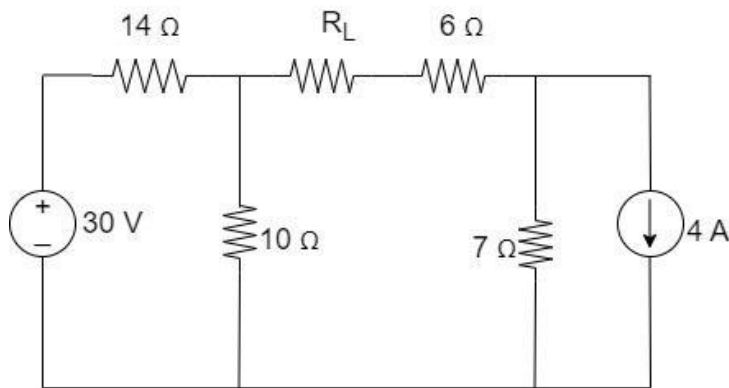


Fig.9

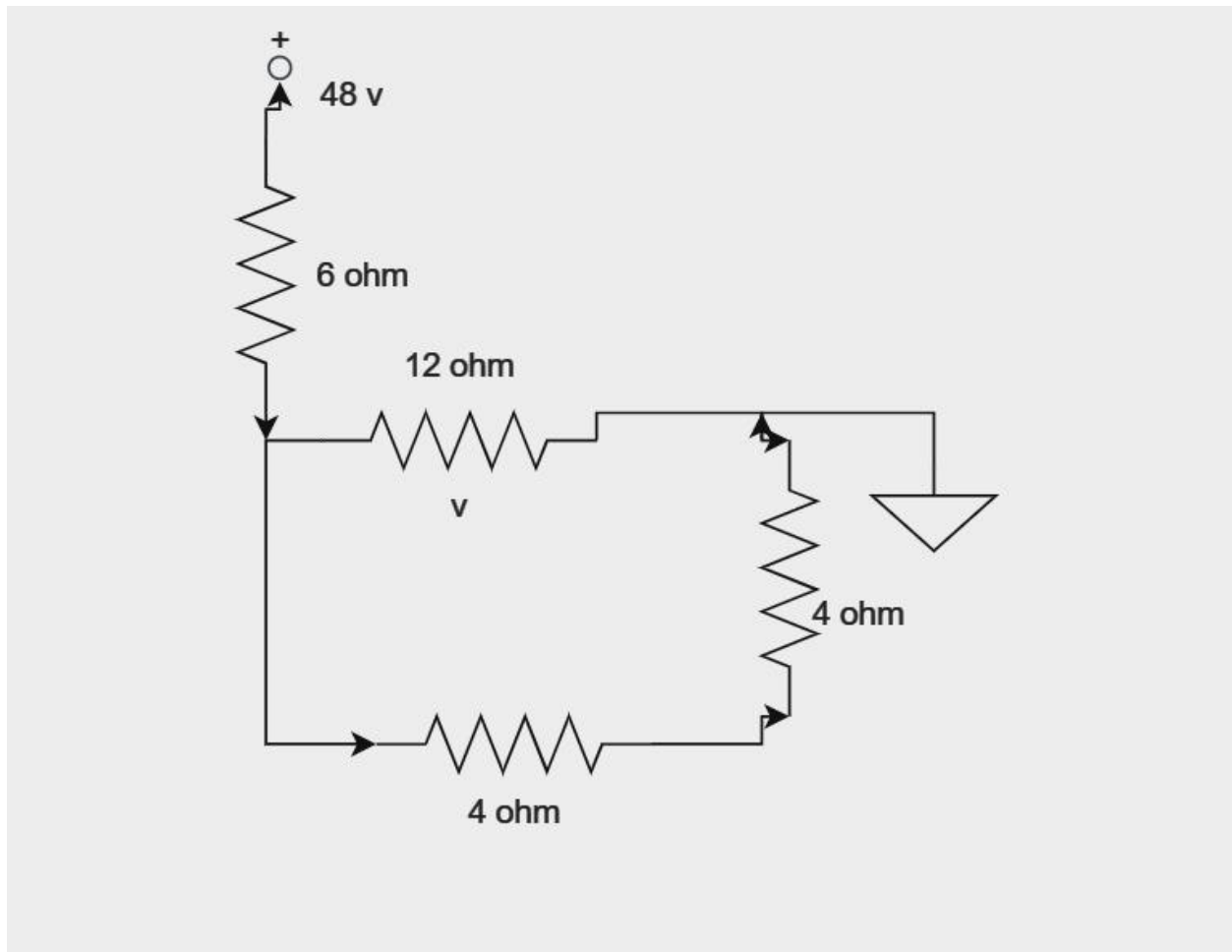10. Find the value of V_{th} and R_{th} between the open terminals A and B of the circuit shown in Fig. 10 [V_{th}=32V, R_{th}=8Ω]



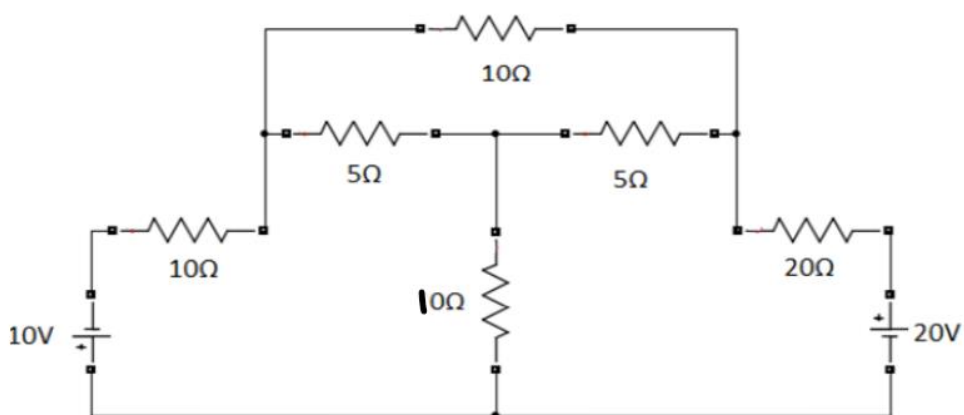11. In the circuit shown in Figure 11, find the power delivered by 10 V source using Node Analysis[ans:11.27w]



12. In the network shown in Fig. 12, calculate the equivalent resistance:

a) between 'A' and 'B' [$R_{th}=4.9468\Omega$]

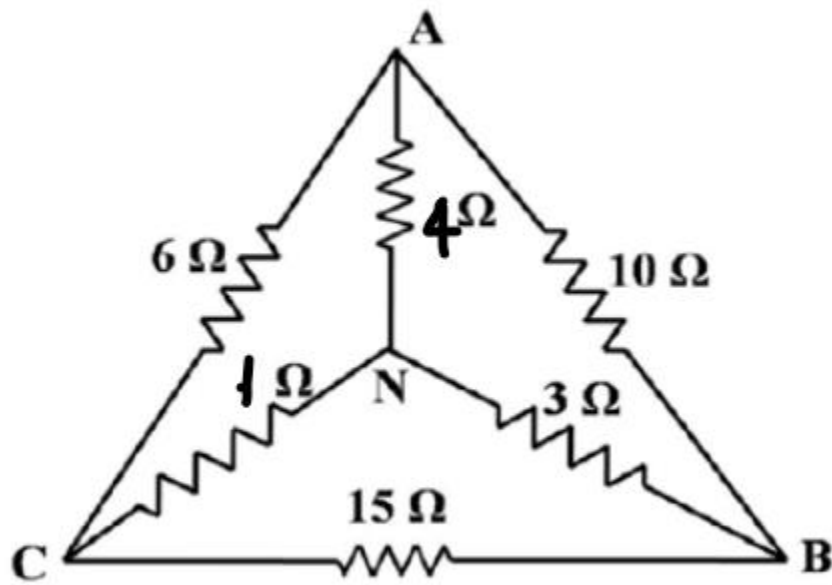


Fig. 12

b) between 'A' and 'N'. [$R_{th}=4.541\Omega$]