

## ET Tutorial Sheet 2

1. A resistance  $R$  is connected in series with an iron core choke coil. The circuit draws a current of 5 A with a source of 240 V, 50 Hz. The voltage across  $R$  and the coil are 120 V and 200 V, respectively. Calculate

(a) the resistance, reactance, and impedance of the coil,

(b) power absorbed in the coil.

(c) power factor of the input current. [Ans: 2.68  $\Omega$ , 39.91  $\Omega$ , 40  $\Omega$ , 66.75 W, 0.556]

2. Find  $V_s$  for the circuit shown in Fig. 2. [Ans: 123 $\angle$ 1.43 $^\circ$ ]

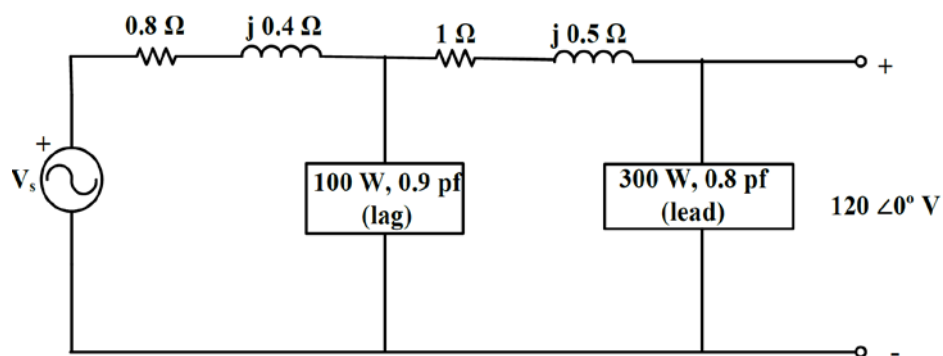


Fig. 2

3. For the circuit shown in Fig. 3, find the current through capacitor using superposition theorem. [Ans: 0.59 $\angle$ 103.3 $^\circ$ ]

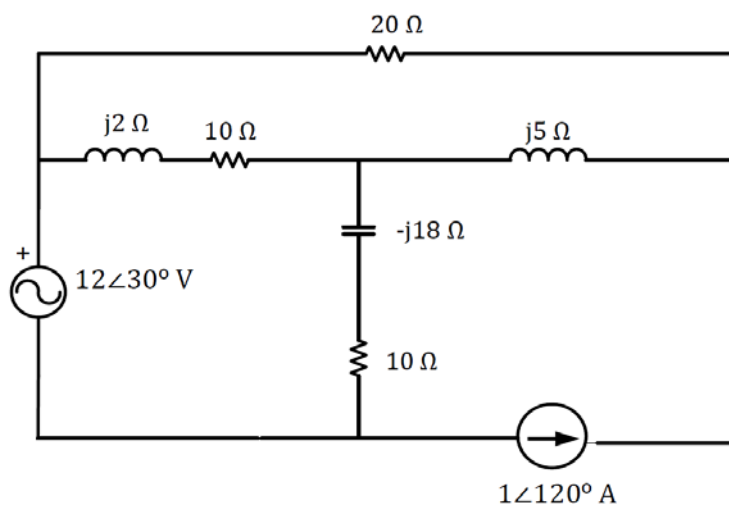


Fig. 3

4. For the circuit shown in Fig. 4, determine  $I_L$  using (i) Thevenin theorem, (ii) Norton theorem.  
[Ans:  $2.26 \angle -9.03^\circ$ ]

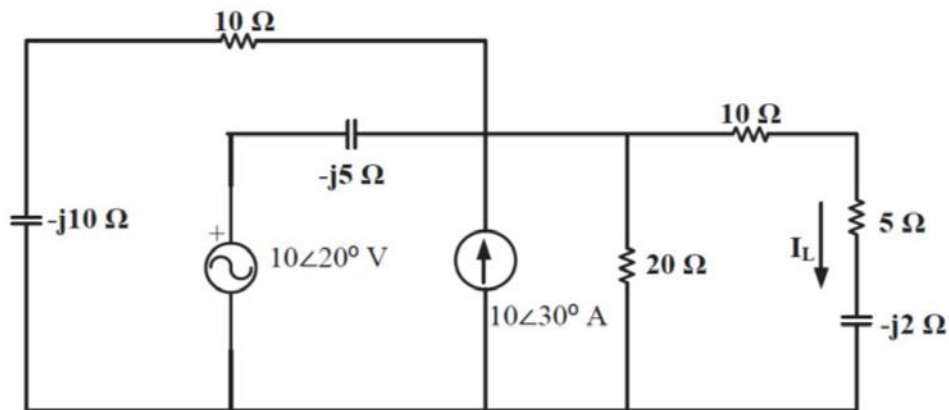


Fig. 4

5. Determine the frequency at which the maximum power is transferred from Block-1 to Block-2, shown in Fig. 5. Also find the maximum delivered power at this frequency if  $V_s = 3.8 \angle 0^\circ$ .  
[Ans: 1.59 kHz, 0.45 W]

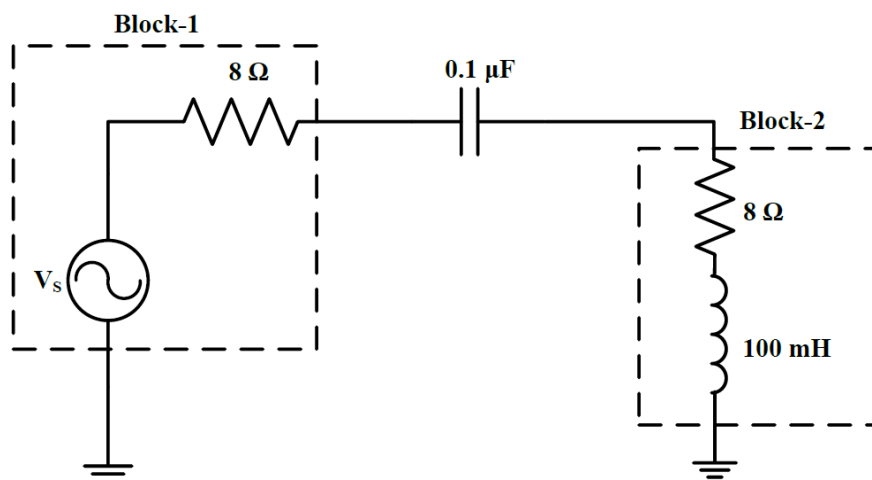


Fig. 5

6. A resistor of  $50 \Omega$  in parallel with an inductor of  $30 \text{ mH}$  is connected in series with a capacitor. A voltage of  $220 \text{ V}$ ,  $50 \text{ Hz}$  is applied to the circuit. Find (a) the value of the capacitor to give unity power factor, (b) the current delivered by the source, and (c) the current in the inductor.  
[Ans:  $349 \mu\text{F}$ ,  $128 \text{ A}$ ,  $125.78 \text{ A}$ ]
7. Determine what value of capacitor in Fig. 6 is required to bring the source power factor up to  $0.85$  (lag). Also find  $I$  before and after the power factor correction. The supply frequency is  $50 \text{ Hz}$ .  
[Ans:  $C=366.5 \mu\text{F}$ ,  $I(\text{before})=328.04 \angle -42.1^\circ \text{ A}$ ,  $I(\text{after})=286.4 \angle -31.8^\circ \text{ A}$ ]

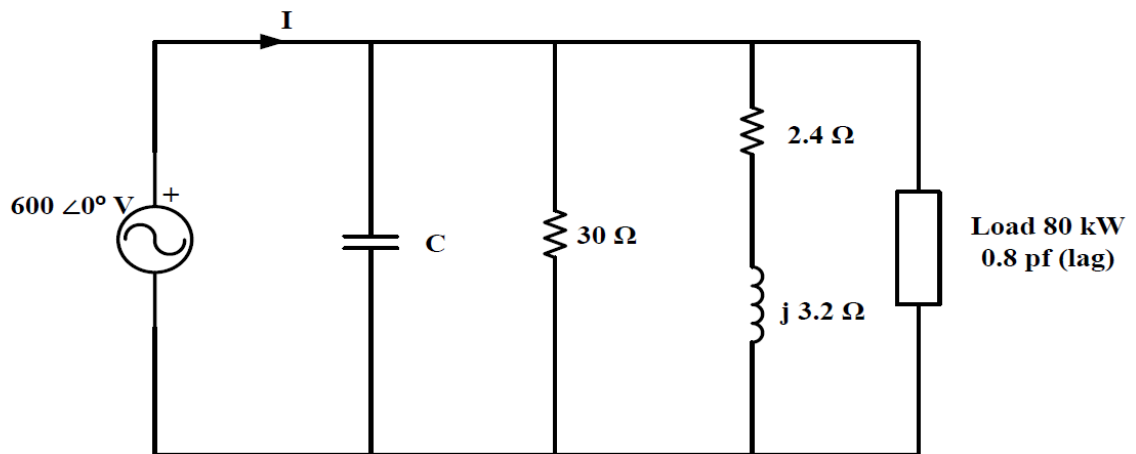


Fig. 6

8. A voltage of 200 V is applied to a series circuit consisting of a resistor, a coil and a capacitor. The respective voltages across these components are 170, 150, and 100 V and the current is 4 A. Find the p.f. of the coil, and of the circuit. Draw a suitable phasor diagram of the circuit. [Ans: 0.16, 0.97]
9. In a series RLC circuit,  $L$  is varied to produce resonance keeping the supply frequency and  $C$  fixed. The circuit contains  $R=100\ \Omega$ , the capacitive reactance  $X_C = 200\ \Omega$ ,  $f = 50\ \text{Hz}$  and the supply is 1000 V. Find the voltage drop across  $L$  at resonance and also when the drop across it is a maximum. [Ans: 2 kV, 2.236 kV]
10. In the circuit of Fig. 7, the switch was open and the circuit was operating at steady state. At  $t = 0$ , the switch is closed. Derive the expression for inductor current  $i(t)$  for  $t > 0$ . [Ans:  $\frac{10}{63}e^{-6t} + \frac{5}{9}\text{ A}$ ]

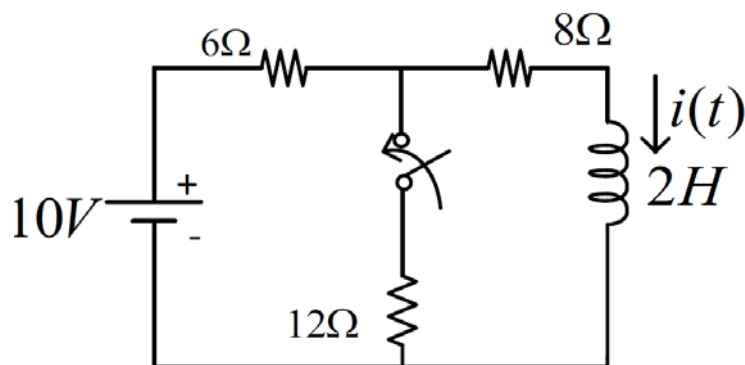


Fig. 7

11. The circuit in Fig. 8 was in steady state and the switch  $S$  was open. At  $t = 0$ , and the switch is closed. Find the expression of the current  $i(t)$  through the inductor of 2 H for  $t > 0$ . [Ans:  $\frac{7}{6} - \frac{1}{6}e^{-12t}\text{ A}$ ]

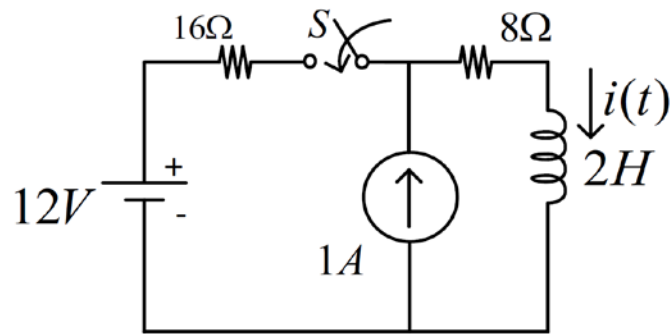


Fig. 8

12. The circuit in Fig. 9 was in steady-state for  $t < 0$ , and the position of the switch is changed at  $t = 0$ . Find the capacitor voltage  $V_c(t)$  and the current  $i(t)$  in the  $100\ \Omega$  resistor for  $t > 0$ .  
 [Ans:  $v_c(t) = \frac{175}{3}e^{-0.8t} + 25\text{ V}$ ,  $i(t) = \frac{7}{12}e^{-0.8t} + \frac{1}{4}\text{ A}$ ]

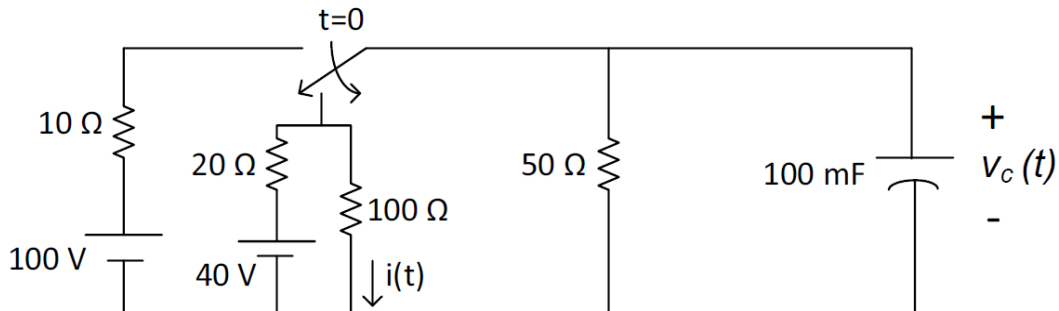


Fig. 9

13. The network of Fig. 10 consists of a current source of value  $I_0$  (a constant), two resistors, and a capacitor. At  $t=0$ , the switch 'K' is opened. For the element values given on the figure, determine  $v_2(t)$  for  $t \geq 0$ .  
 [Ans:  $v_2(t) = I_0(1 - 0.67e^{-2t})\text{ V}$ ]

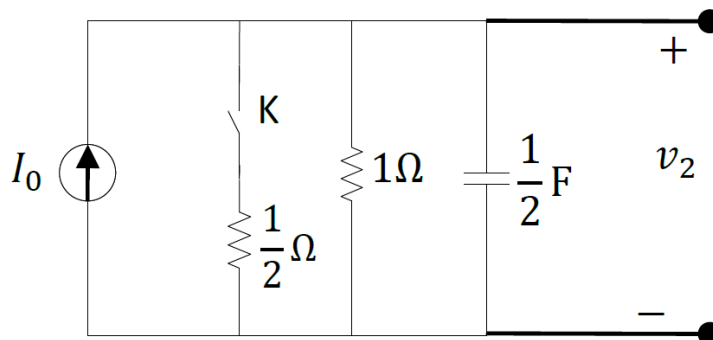


Fig. 10

14. In the network given in Fig. 11, the switch K is opened at  $t=0$ . At  $t=0+$ , solve for the values of  $v$ ,  $\frac{dv}{dt}$ , and  $\frac{d^2v}{dt^2}$  at  $t=0+$  if  $I=10\text{ A}$ ,  $R=1000\Omega$ , and  $C=1\mu\text{F}$ .

[Ans: 0,  $10^7$  V/s,  $-10^{10}$  V/s<sup>2</sup>]

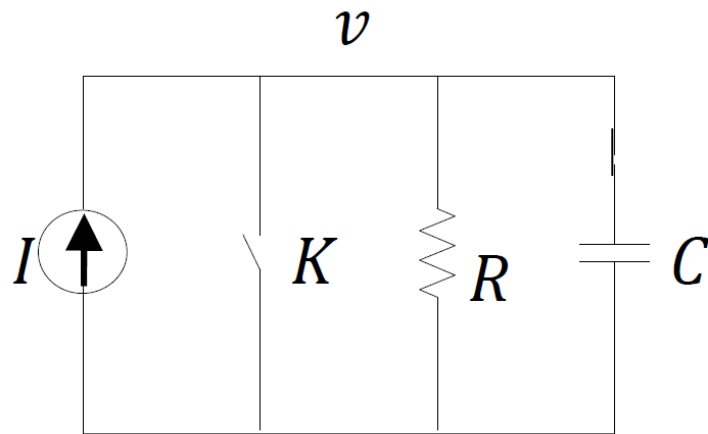


Fig. 11

15. The network shown in Fig. 12 has the switch 'K' opened at  $t = 0$ . Solve for  $v$ ,  $\frac{dv}{dt}$ , and  $\frac{d^2v}{dt^2}$  at  $t=0+$  if  $I=1$  A,  $R=100\ \Omega$ ,  $r=10\ \Omega$ , and  $L=1$  H. [Ans: 100 V,  $-10^4$  V/s,  $10^6$  V/s<sup>2</sup>]

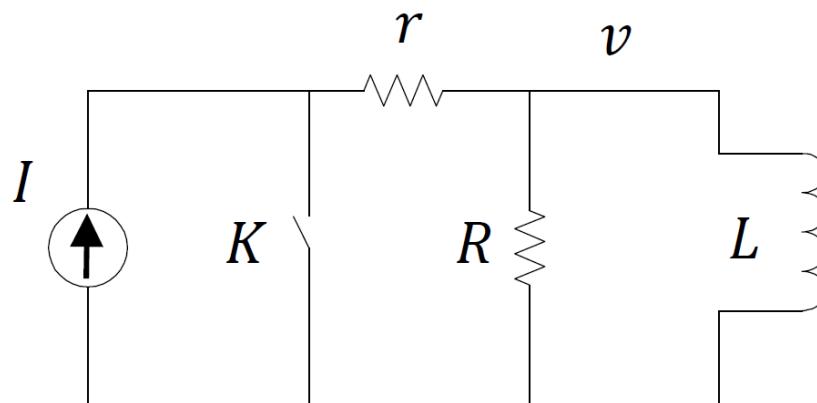


Fig. 12

16. In the circuit shown in Fig. 13, the switch is caused to snap back and forth between the two positions A and B at regular intervals equal to  $L/R$  sec. After a large number of cycles the current becomes periodic, as shown in the accompanying plot. Determine the current levels  $I_1$  and  $I_2$  characterizing this periodic waveform.

[Ans:  $I_1 = \frac{E}{E(1+e)}$ ,  $I_2 = \frac{Ee}{E(1+e)}$ ]

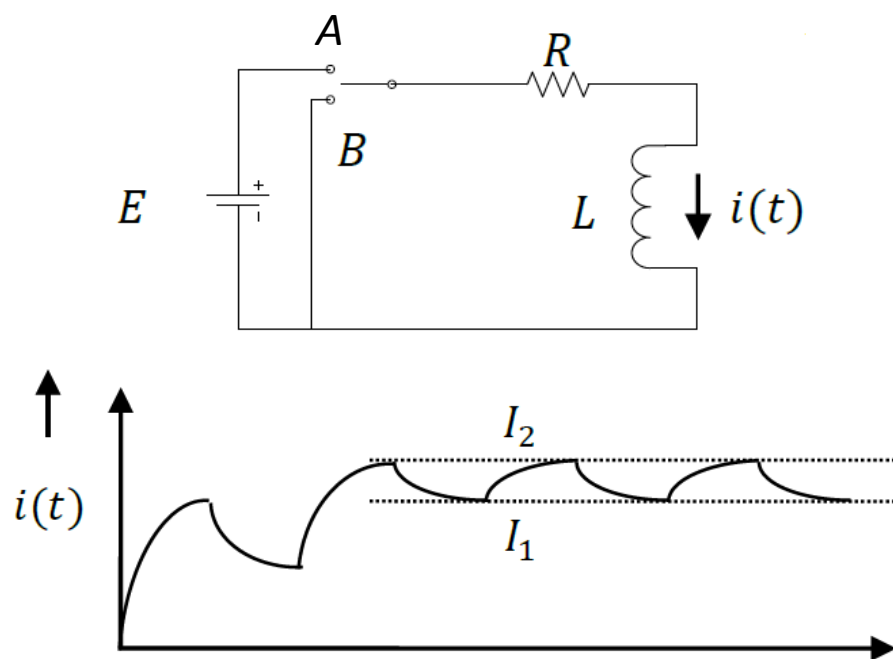


Fig. 13